

www.JetPackAcademy.com

555 MOSFET PWM speed controller

Please note: R5 is different from what is shown in the video lesson. I also made a mistake in the circuit build in the video. This circuit diagram is correct.

