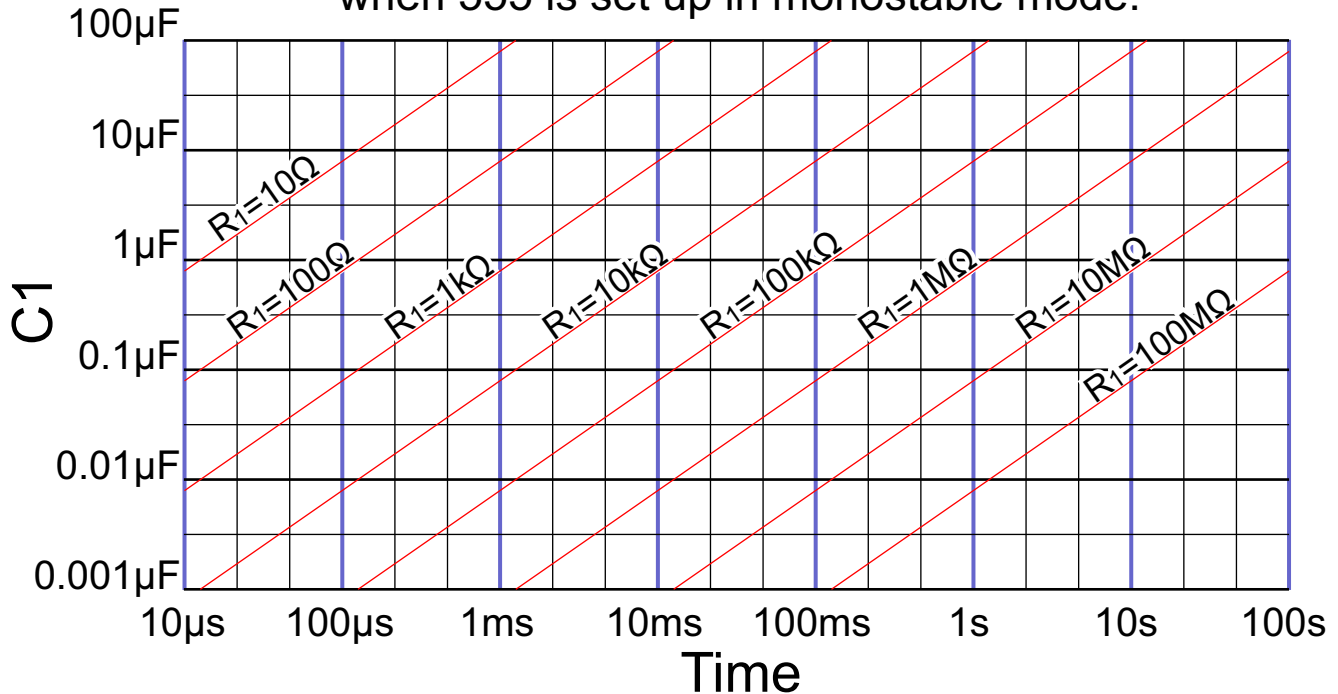




www.JetPackAcademy.com

555 Monostable or “one shot” timer Quick reference sheet

Quick reference chart for pulse duration
when 555 is set up in monostable mode.



The time is calculated $t = 1.1 \times R_1 \times C_1$. R_1 is in ohms, C_1 is in **Farads**.
Example: If $R_1 = 100k$ and $C_1 = 100\mu F$,
 $1.1 \times 100,000 \times 0.0001 = 11$ seconds.

