

www.JetPackAcademy.com

Lightwave telephone

Receiver Receiver will convert any light modulation into Capacitor and resistor from pin 8 to 1 sound. So 60 hz from nearby lights will be picked will distort the sound, but may be needed up. Will also pick up light modulated by to make the gain high enough reflection off of a vibrating surface. Light from the C3 LED on the transmitter is shone on the CDS cell of 220µF the receiver to talk on a lightwave. Use lenses to C4 R2 increase the transmission distance. 10μF R1 100Ω 10k +9V 10μF Transmitter C1 LM386 1μF R1 CDS R3 10k R2 +9V 22k cell 330Ω 13 C1 1 µF 1/4 TL074CN 14 mic **5**11 -9V Note: LED goes to -9V, NOT ground! This holds the LED in forward bias and

the output varies its intensity.